

**FACULTY OF SCIENCE**

**M. Sc. II – Semester Examination, May / June 2018**

**Subject : Physics & Applied Electronics**

**Paper – IV : Electronics**

**Time : 3 Hours**

**Max. Marks: 80**

**Note : Answer all questions from Part–A and Part–B. Each question carries 4 marks in Part–A and 12 marks in Part – B.**

**PART – A (8 x 4 = 32 Marks)**

**(Short Answer Type)**

- 1 Define line regulation, load regulation, temperature coefficient and ripple rejection of a stabilized power supply.
- 2 Explain the concept of feedback and obtain the expression for feedback gain in the case of positive and negative feedback.
- 3 Explain the operational amplifier as a differentiator.
- 4 Draw the circuit diagram counter method A/D converter and describe its operation.
- 5 Explain the writing of Boolean equation for a truth table using product of sums method.
- 6 What is a Multiplexer? Explain the working of 4-to-1 multiplexer with suitable circuit diagram.
- 7 Mention the various status flags provided in 8085? Discuss their role.
- 8 Write an assembly language program for a 8-bit subtraction.

**PART – B (4 x 12 = 48 Marks)**

**(Essay Answer Type)**

- 9 (a) Explain the working of Collpitts oscillator with a neat diagram and obtain the expression for frequency and condition for sustained oscillations.  
**OR**  
(b) What are relaxation oscillators? Explain the construction and working of an astable multivibrator with suitable waveforms and obtain the expression for the time period.
- 10 (a) Discuss the frequency response of a non-inverting amplifier with a neat diagram and deduce the expression for feedback gain, input impedance and output resistance.  
**OR**  
(b) Describe the functioning of a Successive approximation A/D converter and mention its advantages.
- 11 (a) Draw the NAND and NOR RS-Latches and verify their truth tables. How bubbled-latch can be converted into a clocked D-latch? Explain.  
**OR**  
(b) Distinguish asynchronous and synchronous counters. What do you mean by modulus-N-counters? Construct a Mod-10-counter using four JK flip-Flops and explain its operation.
- 12 (a) Draw the block diagram of inter 8085 and explain its architecture in detail.  
**OR**  
(b) What are the addressing modes used in 8085 microprocessor? Explain each one of them with two examples.